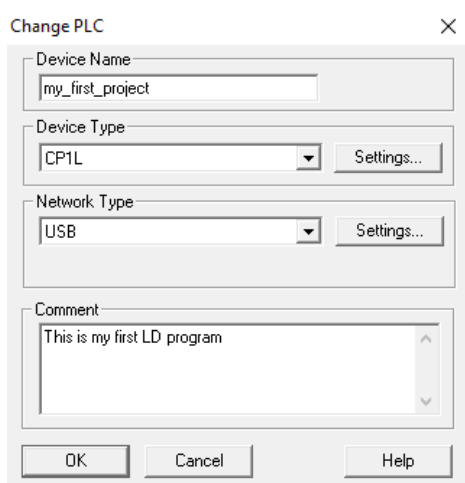




## Exercise no 1: Ladder Diagram Introduction

**Introduction.** Omron *CX-Programmer* is included in *CX-One* which is an integrated package for all of Omron's PLC series. The application includes a wide variety of features to speed up the development of a PLC program. New parameter-setting dialogues reduce setup time, and with standard function blocks in IEC 61131-3 structured text or conventional ladder language

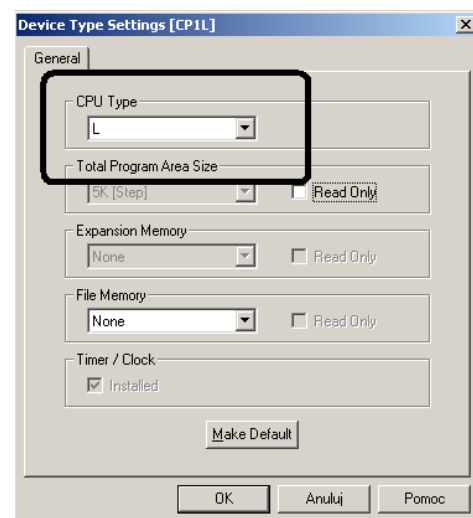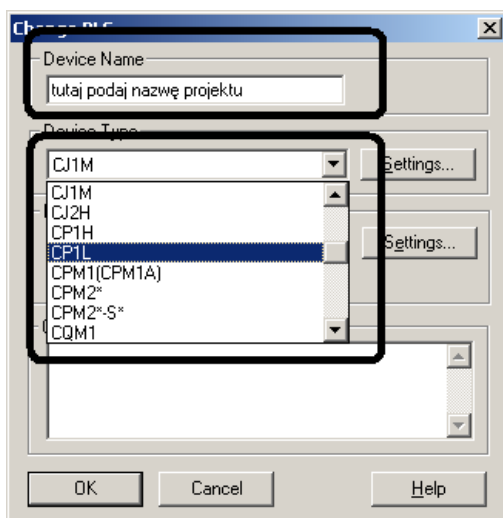**Task.1.** Run *CX-Programmer*. From the *File* menu choose *New...* (*File*→*New...*).




- *Device Name* - the name of the project.
- *Device Type* - PLC type that is used in the project.
- *Network Type* - the interface between PC and PLC.
- *Comment* - designer notes.




## Exercise no 1: Ladder Diagram Introduction

Create the following application:

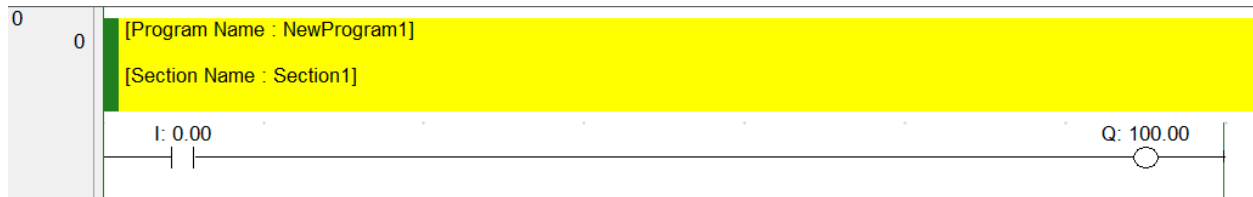


From the *Simulation* menu choose *Work Online Simulator* (*Simulation*→*Work Online Simulator*). Wait for the gray background. Use the simulator to see how the program works.

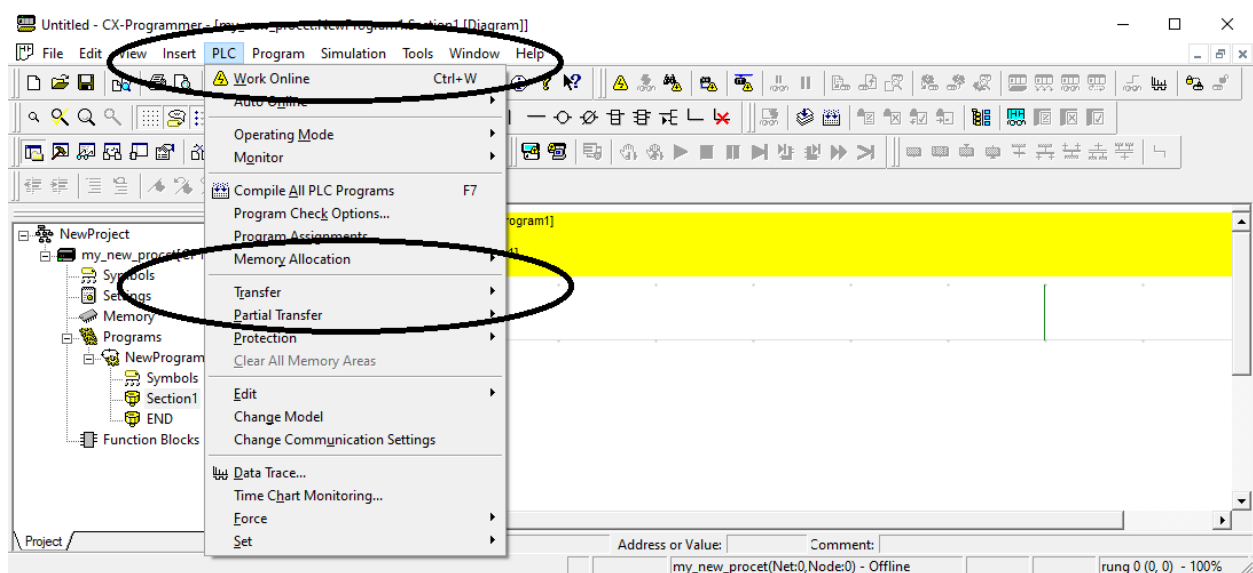Close the simulator (*Simulation*→*Work Online Simulator*). Send this program to the PLC using the combination: *PLC* → *Work Online*; *PLC* → *Transfer* → *To PLC...*




## Exercise no 1: Ladder Diagram Introduction

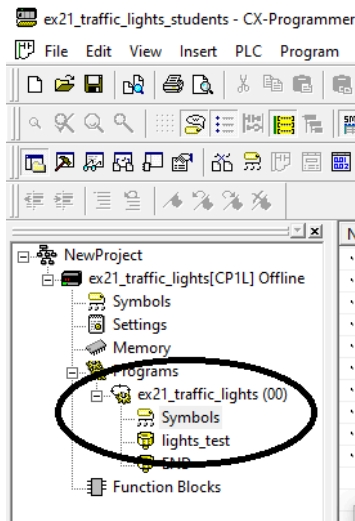**Task.2.** Run *CX-Programmer*. From the *File* menu choose *New...* (*File*→*New...*).




In the project tree, open the *Programs* tab. Select *Symbols*.

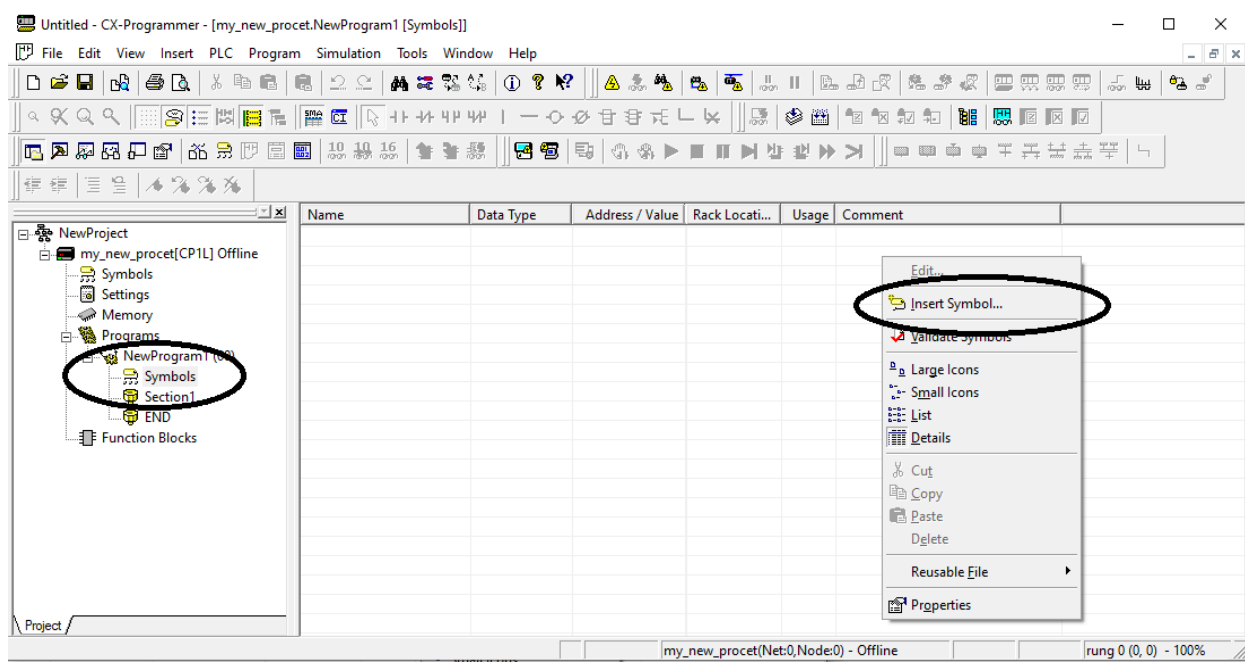Press the right mouse button while keeping the mouse pointer inside the *Symbols* window. Select *Insert Symbol*.


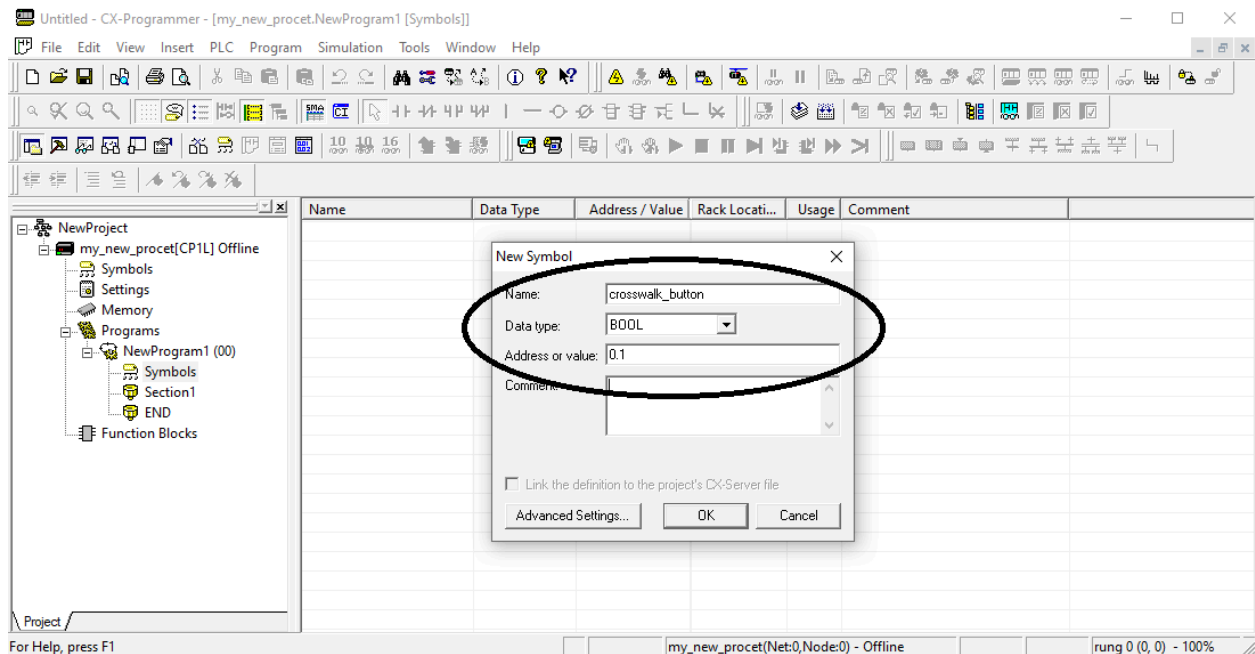
## Exercise no 1: Ladder Diagram Introduction

Enter the *Name* and address in the PLC memory (*Address or value*).




Create symbols according to the following table:

Hardware	Input symbol	Input	Output symbol	Output
Omron #1	button_1	0.0	out_1	100.0
	button_2	0.1	out_2	100.1
	button_3	0.2	out_3	100.2
Omron #2	button_1	0.0	out_1	100.0
	button_2	0.2	out_2	100.1
	button_3	0.3	out_3	100.2
Omron #3	button_1	0.0	out_1	100.0
	button_2	0.2	out_2	100.1
	button_3	0.4	out_3	100.2

## Exercise no 1: Ladder Diagram Introduction

Omron #4	button_1	0.0	out_1	100.0
	button_2	0.1	out_2	100.2
	button_3	0.3	out_3	100.3

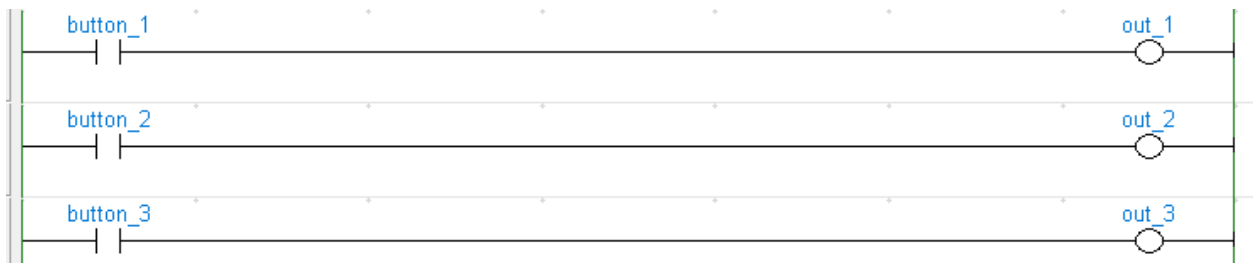**Task.3.** Using symbols from Task 2 build the following LD diagram in the *CX-Programmer*.



Send this program to the PLC. Check if it works.

**Task.4.** Using symbols from Task 2 build the following LD diagram in the *CX-Programmer*. Send this program to the PLC. Check if it works.



**Task.5.** Using symbols from Task 2 build the following LD diagram in the *CX-Programmer*. Send this program to the PLC. Check if it works.




## Exercise no 1: Ladder Diagram Introduction

**Task.6.** Using symbols from Task 2 build the following LD diagram in the *CX-Programmer*. Send this program to the PLC. Check if it works.



**Task.7.** Using symbols from Task 2 build the following LD diagram in the *CX-Programmer*. Send this program to the PLC. Check if it works.

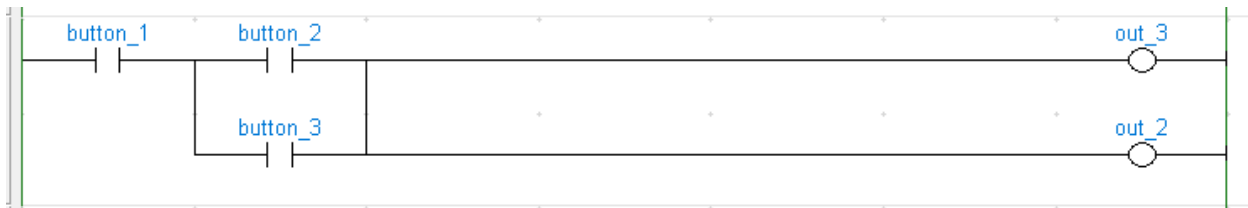


**Task.8.** Using symbols from Task 2 build the following LD diagram in the *CX-Programmer*. Send this program to the PLC. Check if it works.



## Exercise no 1: Ladder Diagram Introduction

---

**Task.9.** Using symbols from Task 2 build the following LD diagram in the *CX-Programmer*. Send this program to the PLC. Check if it works.

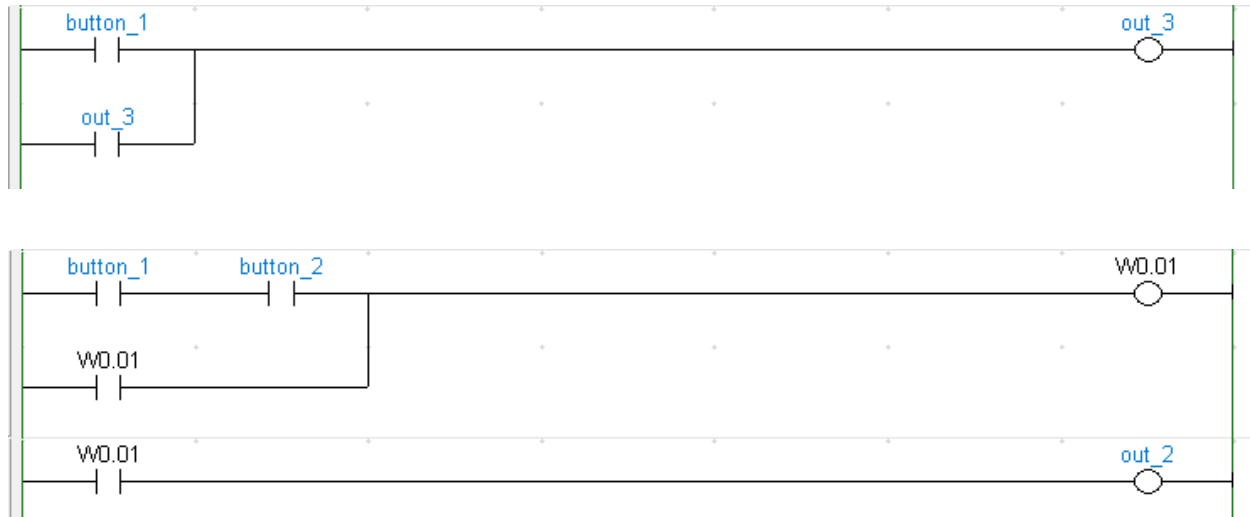

**Task.10.** Using symbols from Task 2 prepare a solution that meets the following parameters:

1.  $out\_1 = button\_1 \mid button\_2$ ;
2.  $out\_2 = out\_1 \& button\_3$ ;
3.  $out\_2$  should be energized, even when the input ceases.

The prepared program should be sent to the PLC and its operation presented to the teacher. After completing the task, the cxp file should be sent to the e-mail address shown in the footer, along with the authors of the solution.

**Task.11.** Using defined symbols prepare a solution that meets the following parameters:



1. turn on and hold (latch)  $out\_3$  if  $button\_3$  and  $button\_1$  were pressed;
2. turn on  $out\_3$  if  $button\_2$  and  $button\_3$  were pressed.

## Exercise no 1: Ladder Diagram Introduction

**Task.12. KEEP** function. Add a new symbol.

Hardware	Input symbol	Input
Omron #1	button_4	0.3
Omron #2		0.1
Omron #3		0.1
Omron #4		0.2

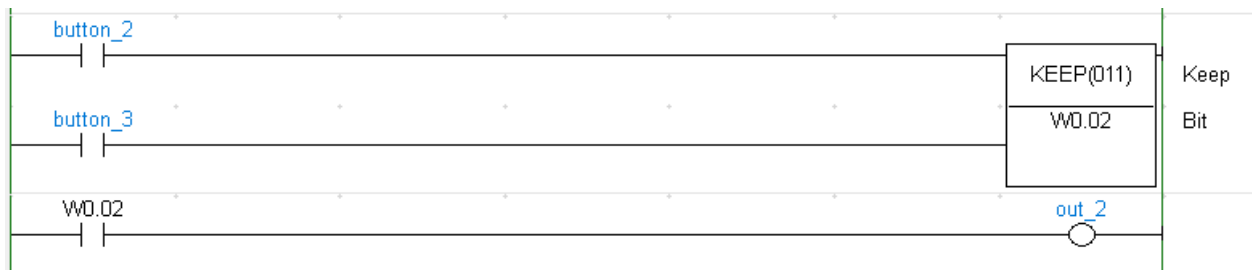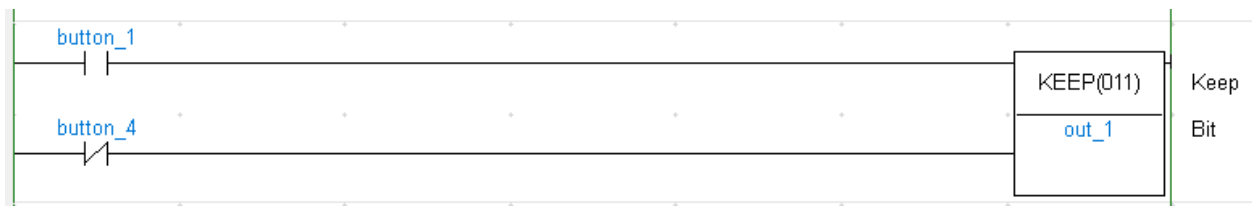Build the following LD diagrams. Check the results.






## Exercise no 1: Ladder Diagram Introduction

**Task.13. SET/RSET** function. Build the following LD diagrams. Check the results.



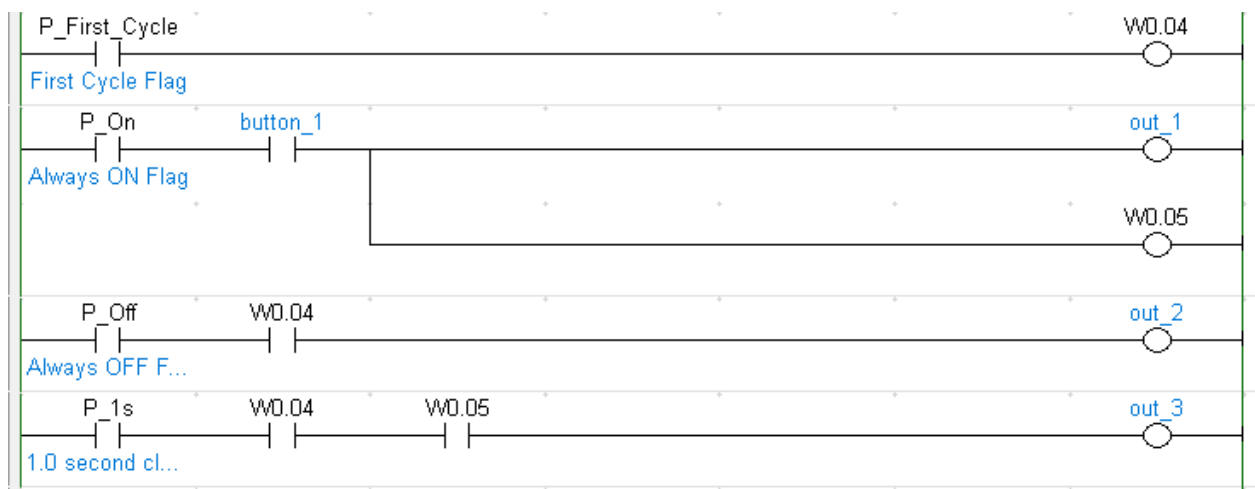**Task.14. P** flags. Build the following LD diagrams. Check the results.




## Exercise no 1: Ladder Diagram Introduction

**Task.15. Timer.** Build the following LD diagrams. Check the results.

Timer function syntax: **TIM 1 #100**




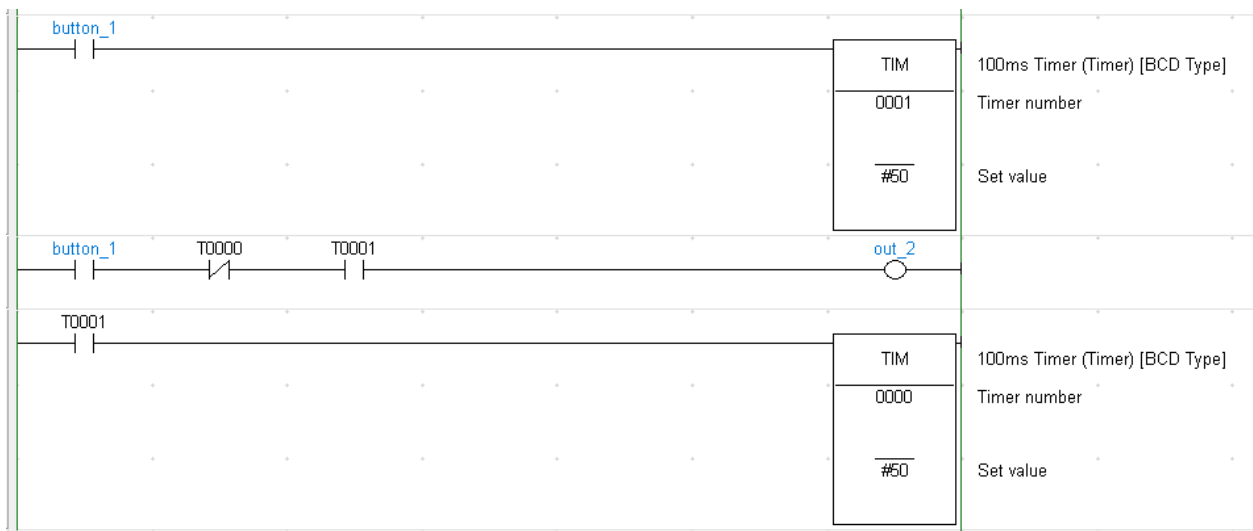**Task.16.** Build the following LD diagram. Check the results.



## Exercise no 1: Ladder Diagram Introduction

**Task.17.** Build the following LD diagram. Check the results.

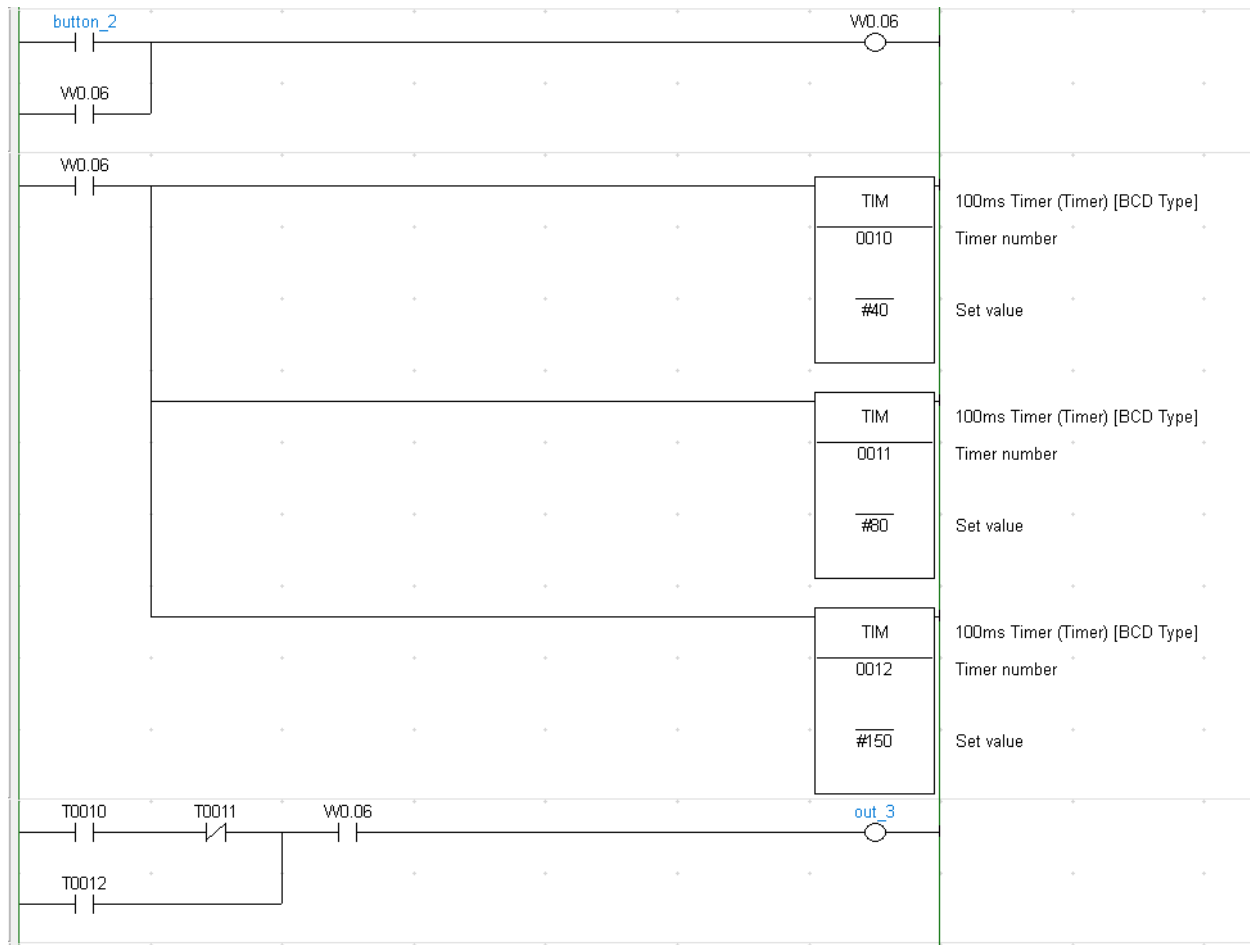

**Task.18.** Generate a 4s pulse on `out_2`, triggered by pressing the `button_3`.

**Task.19.** Generate 2 5s pulses on `out_1` triggered by pressing the `button_1`. The second pulse should be generated 10s after the first pulse is completed.

**Task.20.** Prepare a solution that meets the following parameters:

1. `out_1` is energized (on) 5s after either `button_1` or `button_2` is pressed.
2. `out_2` is energized (on) 3s after `button_1` and `button_2` were pressed.

3. *button\_3* resets the system.

**Task.21.** Create an LD program that produces a 2Hz 50% PWM signal on *out\_2*.

**For those interested:**

1. CX-Programmer Introduction Guide:

[www.fa.omron.com.cn/data\\_pdf/mnu/r132-e1-05\\_cx-programmer.pdf?id=1605](http://www.fa.omron.com.cn/data_pdf/mnu/r132-e1-05_cx-programmer.pdf?id=1605)

2. CP1L Programming Manual:

[assets.omron.eu/downloads/manual/en/v1/w451\\_cp1\\_cpu\\_unit\\_programming\\_manual\\_en.pdf](http://assets.omron.eu/downloads/manual/en/v1/w451_cp1_cpu_unit_programming_manual_en.pdf)